

Mini Project

Verilog code:

```

1  module project (A,B,C,BCIN,D,CARRYIN,M,P,CARRYOUT,CARRYOUTF,CLK,OPMODE,CEA,CEB,CECARRYIN,CEC,CED,CEM,CEOPMODE,CEP,RSTA,RSTB,RSTC,RSTCARRYIN,RSTD,RST
2  parameter A0REG = 0 ;
3  parameter A1REG = 1 ;
4  parameter B0REG = 0 ;
5  parameter B1REG = 1 ;
6  parameter CREG=0, DREG=0, MREG=0,PREG=0, CARRYINREG=0, CARRYOUTREG=0,OPMODEREG = 0 ;
7  parameter CARRYINSEL = "OPMODE5";
8  parameter B_INPUT = "DIRECT" ;
9  parameter RSTTYPE = "SYNC" ;
10 input [17:0] A,B,D,BCIN ;
11 input [47:0] C,PCIN;
12 input [7:0] OPMODE ;
13 input CARRYIN,CLK,CEA,CEB,CEC,CECARRYIN,CED,CEM,CEOPMODE,CEP ;
14 input RSTA,RSTB,RSTC,RSTCARRYIN,RSTD,RSTM,RSTOPMODE,RSTP ;
15 output [35:0] M ;
16 output [47:0] P ;
17 output CARRYOUTF,CARRYOUT ;
18 output [17:0] BCOUT ;
19 output [47:0] PCOUT ;
20 wire [17:0] W1,W22,W3,W4,W5,W6,W10,W2;
21 wire [47:0] W7,CON,MMUX,W15;
22 reg [47:0] W11,W14 ;
23 wire [35:0] W8,W9;
24 wire[1:0] OP,OP2 ;
25 wire W12,W13,W16,W17 ;
26 assign W17 = (RSTTYPE=="SYNC") ? 1 : 0 ; //we should sent W12 to any muxreg instantiation when we need to change from sync to asuncrous but know as
27 muxreg m1(D,CLK,DREG,RSTD,CED,W1) ;
28 muxreg m2(B,CLK,B0REG,RSTB,CEB,W22) ;
29 assign W2 = (B_INPUT == "DIRECT") ? W22 : (B_INPUT == "CASCADE") ? BCIN : 0 ;
30 ADDER A1(W1,W2,OPMODE[6],W3) ;
31 assign W10 = (OPMODE[4]==1) ? W3:W2 ;
32 muxreg m3(W10,CLK,B1REG,RSTB,CEB,W4) ;
33 assign BCOUT = W4 ;
34 muxreg m4(A,CLK,A0REG,RSTA,CEA,W5) ;
35 muxreg m5(W5,CLK,A1REG,RSTA,CEA,W6) ;
36 muxreg #(.size(48))m6(C,CLK,CREG,RSTC,CEC,W7) ;
37 assign W8 = W4*W6 ;
38 muxreg #(.size(36))m7(W8,CLK,MREG,RSTM,CEM,W9) ;
39 assign M = W9 ;
40 assign CON = {D[11:0], A[17:0], B[17:0]};
41 assign MMUX = {12'b000000000000,M} ;
42 assign OP = OPMODE[1:0] ;
43 always @(*) begin
44     case (OP)
45         2'b00 : W11 = 0 ;
46         2'b01 : W11 = MMUX ;
47         2'b10 : W11 = P ;
48         2'b11 : W11 = CON ;
49     endcase
50 end
51 assign W12 = (CARRYINSEL=="OPMODE5") ? OPMODE[5] : (CARRYINSEL=="CARRYIN") ? CARRYIN : 0 ;
52 muxreg #(.size(1))m8(W12,CLK,CARRYINREG,RSTCARRYIN,CECARRYIN,W13) ;
53 assign OP2 = OPMODE[3:2] ;
54 always @(*) begin
55     case (OP2)
56         2'b00 : W14 = 0 ;
57         2'b01 : W14 = PCIN ;
58         2'b10 : W14 = P ;
59         2'b11 : W14 = W7 ;
60     endcase
61 end
62 post A2(W14,W11,W13,OPMODE[7],W15,W16) ;
63 muxreg #(.size(48))m9(W15,CLK,PREG,RSTP,CEP,P) ;
64 assign PCOUT = P ;
65 muxreg #(.size(1))m10(W16,CLK,CARRYOUTREG,RSTCARRYIN,CECARRYIN,CARRYOUT) ;
66 assign CARRYOUTF = CARRYOUT ;
67
68
69
70 endmodule

```

Pre Adder module:

```
module ADDER (in1,in2,op,out);  
parameter siz = 18 ;  
input [siz-1:0] in1,in2 ;  
input op ;  
output reg [siz-1: 0] out ;  
always @(*) begin  
    if(op)  
        out = in1-in2 ;  
    else  
        out = in1+in2 ;  
end  
  
endmodule
```

Post adder module:

```
module post (in1,in2,cin,opcode,out,cout);  
input [47:0] in1,in2 ;  
input cin,opcode ;  
output reg [47:0] out ;  
output reg cout ;  
always @(*) begin  
    if (opcode) begin  
        out = in1 -(in2+cin) ;  
    end  
    else begin  
        {cout,out} = in1 + in2 + cin ;  
    end  
end  
  
endmodule
```

Mux register module:

```
module muxreg (in,clk,select,reset,clk_en,q);
    parameter size = 18 ;
    parameter RSTYPE = 1 ;
    input select,reset,clk_en ;
    input clk ;
    input [size-1:0] in ;
    output [size-1:0] q ;
    reg [size-1:0] wire1 ;
    generate
    if(RSTYPE)begin

        always @(posedge clk) begin
            if (reset)
                wire1=0 ;

            else
                if(clk_en)
                    wire1 = in ;

        end
        assign q = (select==1) ? wire1: in ;
    end
    else begin
        always @(posedge clk or posedge reset) begin
            if (reset)
                wire1=0 ;

            else
                if(clk_en)
                    wire1 = in ;

        end
        assign q = (select==1) ? wire1: in ;
    end
endgenerate
```

Testbench:

```

1  module project tb ();
2  reg [17:0] A_tb,B_tb,D_tb,BCIN_tb ;
3  reg [47:0] C_tb,PCIN_tb ;
4  reg [7:0] OPMODE_tb ;
5  reg CARRYIN_tb,CLK,CEA_tb,CEB_tb,CEC_tb,CECARRYIN_tb,CED_tb,CEM_tb,CEOPMODE_tb,CEP_tb ;
6  reg RSTA_tb,RSTB_tb,RSTC_tb,RSTCARRYIN_tb,RSTD_tb,RSTM_tb,RSTOPMODE_tb,RSTP_tb ;
7  wire [35:0] M_tb ;
8  wire [47:0] P_tb ;
9  wire CARRYOUTF_tb,CARRYOUT_tb ;
10 wire [17:0] BCOUT_tb ;
11 wire [47:0] PCOUT_tb ;
12 project DUT(A_tb,B_tb,C_tb,BCIN_tb,D_tb,CARRYIN_tb,M_tb,P_tb,CARRYOUT_tb,CARRYOUTF_tb,CLK,OPMODE_tb,CEA_tb,CEB_tb,CECARRYIN_tb,CEC_tb,CED_tb,CEM_tb,CEP_tb);
13 initial begin
14     CLK = 0 ;
15     forever begin
16         #10 CLK = ~CLK ;
17     end
18 end
19 initial begin
20     RSTA_tb = 1 ;
21     RSTB_tb = 1 ;
22     RSTC_tb = 1 ;
23     RSTCARRYIN_tb = 1 ;
24     RSTD_tb = 1 ;
25     RSTM_tb = 1 ;
26     RSTOPMODE_tb = 1 ;
27     RSTP_tb = 1 ;
28     CARRYIN_tb = 0 ;
29     CEA_tb = 1 ;
30     CEB_tb = 1 ;
31     CEC_tb = 1 ;
32     CECARRYIN_tb = 1 ;
33     CED_tb = 1 ;
34     CEM_tb = 1 ;
35     CEOPMODE_tb = 1 ;
36     CEP_tb = 1 ;
37     A_tb = 5 ;

```

```


37     A_tb = 5 ;
38     B_tb = 10 ;
39     C_tb = 1 ;
40     D_tb = 7 ;
41     BCIN_tb = 0 ;
42     PCIN_tb = 0 ;
43     OPMODE_tb = 8'b00011110 ;
44     repeat(10) @(negedge CLK) ;
45     RSTA_tb = 0 ;
46     RSTB_tb = 0 ;
47     RSTC_tb = 0 ;
48     RSTCARRYIN_tb = 0 ;
49     RSTD_tb = 0 ;
50     RSTM_tb = 0 ;
51     RSTOPMODE_tb = 0 ;
52     RSTP_tb = 0 ;
53     CARRYIN_tb = 0 ;
54     CEA_tb = 1 ;
55     CEB_tb = 1 ;
56     CEC_tb = 1 ;
57     CECARRYIN_tb = 1 ;
58     CED_tb = 1 ;
59     CEM_tb = 1 ;
60     CEOPMODE_tb = 1 ;
61     CEP_tb = 1 ;
62     A_tb = 5 ;
63     B_tb = 10 ;
64     C_tb = 1 ;
65     D_tb = 7 ;
66     BCIN_tb = 0 ;
67     PCIN_tb = 0 ;
68     OPMODE_tb = 8'b00011101 ;
69     repeat(10) @(negedge CLK) ;
70     RSTA_tb = 0 ;
71     RSTB_tb = 0 ;


```


```
71     RSTB_tb = 0 ;
72     RSTC_tb = 0 ;
73     RSTCARRYIN_tb = 0;
74     RSTD_tb = 0 ;
75     RSTM_tb = 0 ;
76     RSTOPMODE_tb = 0 ;
77     RSTP_tb = 0 ;
78     CARRYIN_tb = 0;
79     CEA_tb = 1 ;
80     CEB_tb = 1 ;
81     CEC_tb = 1 ;
82     CECARRYIN_tb = 1 ;
83     CED_tb = 1 ;
84     CEM_tb = 1 ;
85     CEOPMODE_tb = 1 ;
86     CEP_tb = 1 ;
87     A_tb = 11 ;
88     B_tb = 30 ;
89     C_tb = 87 ;
90     D_tb = 9 ;
91     BCIN_tb = 5 ;
92     PCIN_tb = 6 ;
93     OPMODE_tb = 8'b00011101 ;
94     repeat(10) @(negedge CLK)      ;
95     | RSTA_tb = 0 ;
96     RSTB_tb = 0 ;
97     RSTC_tb = 0 ;
98     RSTCARRYIN_tb = 0;
99     RSTD_tb = 0 ;
100    RSTM_tb = 0 ;
101    RSTOPMODE_tb = 0 ;
102    RSTP_tb = 0 ;
103    CARRYIN_tb = 1;
104    CEA_tb = 1 ;
105    CEB_tb = 1 ;
106    CEC_tb = 1 ;
107    CECARRYIN_tb = 1 ;
108    CED_tb = 1 ;
109    CEM_tb = 1 ;
110    CEOPMODE_tb = 1 ;
111    CEP_tb = 1 ;
112    A_tb = 5 ;
113    B_tb = 10 ;
```

```
114     C_tb = 1 ;
115     D_tb = 7 ;
116     BCIN_tb = 0 ;
117     PCIN_tb = 0 ;
118     OPMODE_tb = 8'b00011111 ;
119     repeat(10) @(negedge CLK) ;
120     | RSTA_tb = 0 ;
121     RSTB_tb = 0 ;
122     RSTC_tb = 0 ;
123     RSTCARRYIN_tb = 0;
124     RSTD_tb = 0 ;
125     RSTM_tb = 0 ;
126     RSTOPMODE_tb = 0 ;
127     RSTP_tb = 0 ;
128     CARRYIN_tb = 1;
129     CEA_tb = 1 ;
130     CEB_tb = 1 ;
131     CEC_tb = 1 ;
132     CECARRYIN_tb = 1 ;
133     CED_tb = 1 ;
134     CEM_tb = 1 ;
135     CEOPMODE_tb = 1 ;
136     CEP_tb = 1 ;
137     A_tb = 5 ;
138     B_tb = 10 ;
139     C_tb = 1 ;
140     D_tb = 7 ;
141     BCIN_tb = 0 ;
142     PCIN_tb = 0 ;
143     OPMODE_tb = 8'b00010101 ;
144     repeat(10) @(negedge CLK) ;
145     $stop ;
146 end
147 endmodule
148
```

RTL:

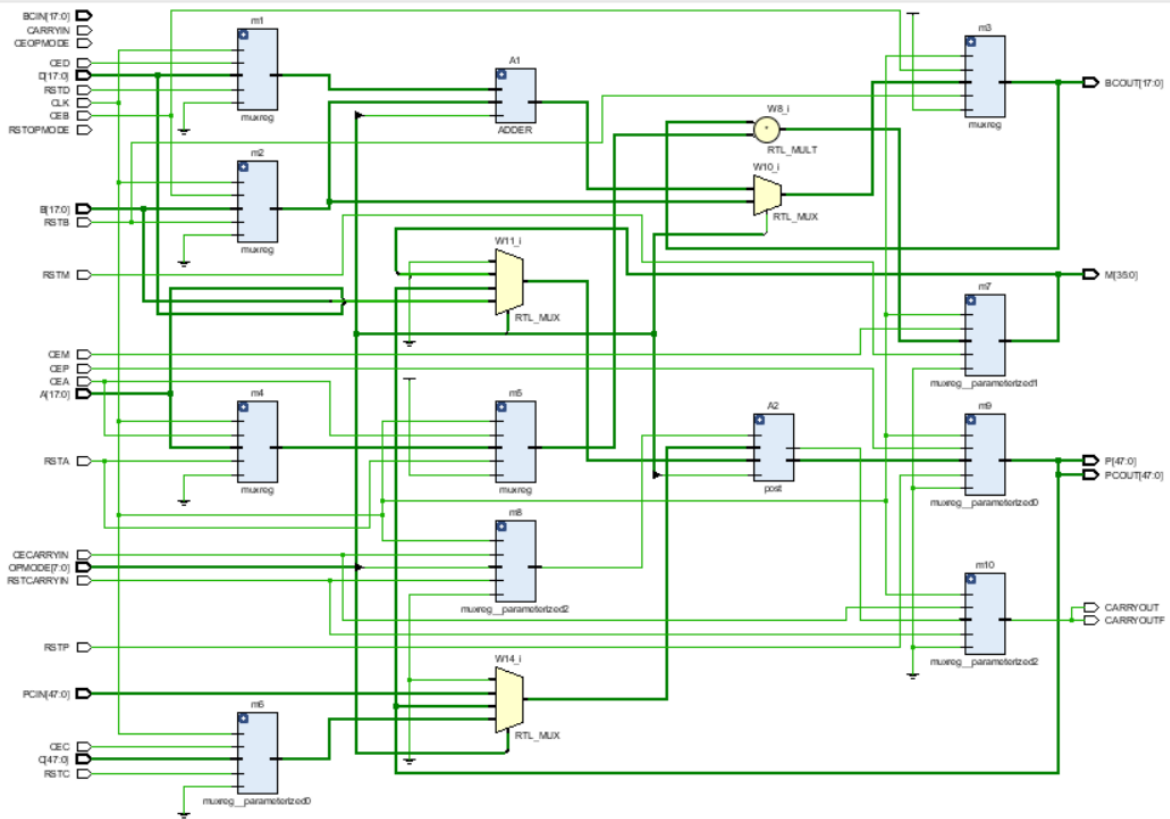

 

 

Utilization report:

Reports

Design Runs

Power

DRC

Methodology

Timing

Utilization

×

Q

≡

⌵

%


Hierarchy

Name	Slice LUTs (303600)	Slice Registers (607200)	Slice (75900)	LUT as Logic (303600)	DSP s (2800)	Bonded IOB (600)	BUFGCTRL (32)
<div> <div>▼</div> <div>N project</div> </div>	340	20	95	340	1	315	2
<div> <div>ⓘ</div> <div>A2 (post)</div> </div>	305	1	79	305	0	0	0
<div> <div>ⓘ</div> <div>m3 (muxreg)</div> </div>	33	18	15	33	0	0	0
<div> <div>ⓘ</div> <div>m5 (muxreg_0)</div> </div>	0	1	1	0	0	0	0

Timing report:

Setup	Hold	Pulse Width
Worst Negative Slack (WNS): inf	Worst Hold Slack (WHS): inf	Worst Pulse Width Slack (WPWS): 4.600 ns
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): 0.000 ns
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: 0
Total Number of Endpoints: 269	Total Number of Endpoints: 269	Total Number of Endpoints: 20
All user specified timing constraints are met.		

Waveform:

 

Name	Waveform	Period (ns)	Frequency (MHz)
sys_clk_pin	{0.000 5.000}	10.000	100.000